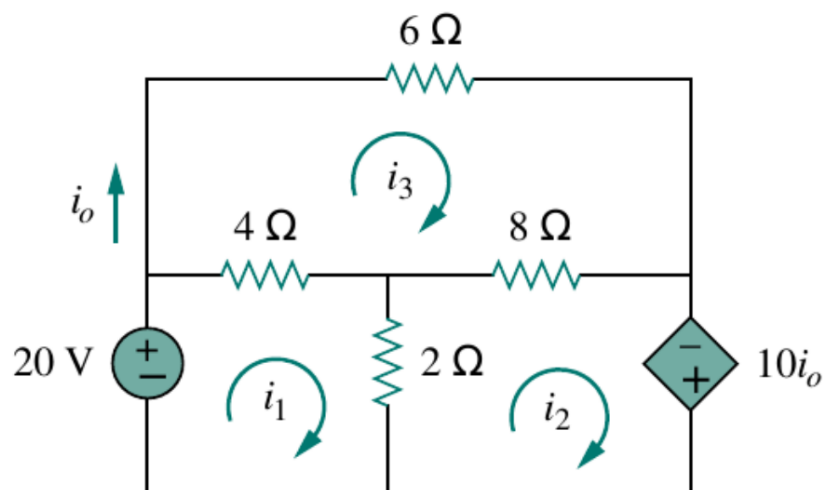



Name _____ Number _____

Signature _____


1 - Using mesh analysis, find i_o in the given circuit (write all mesh equations to obtain full point)



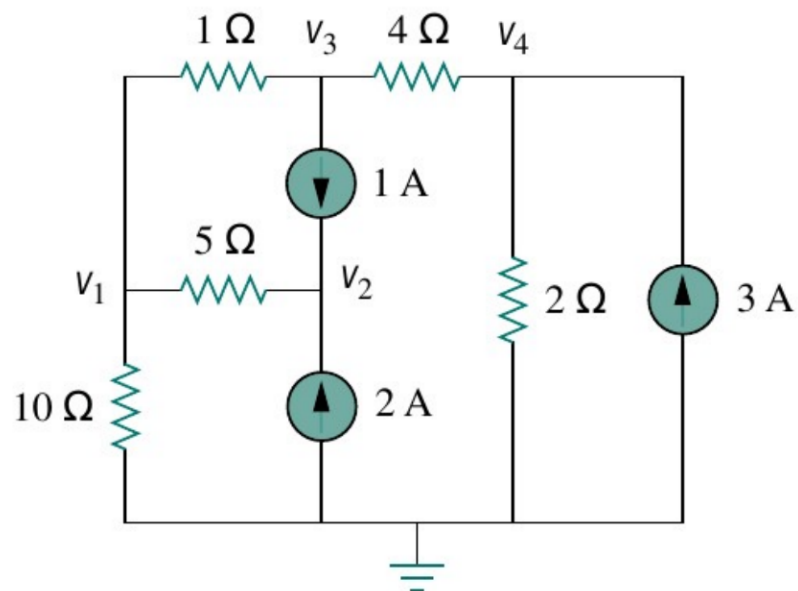
2 - Obtain the node voltage equations, in matrix form, for the circuit given below



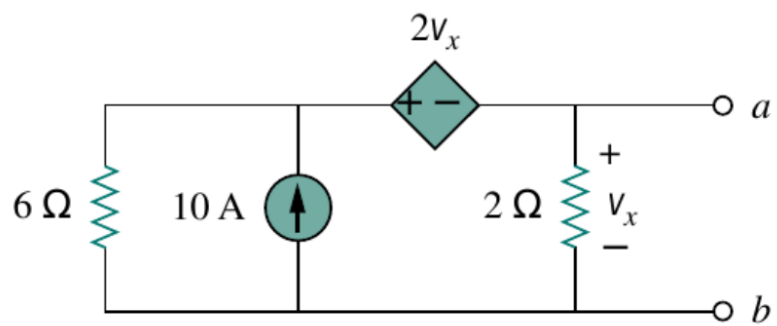3 – Find the Norton equivalent circuit for the circuit given below



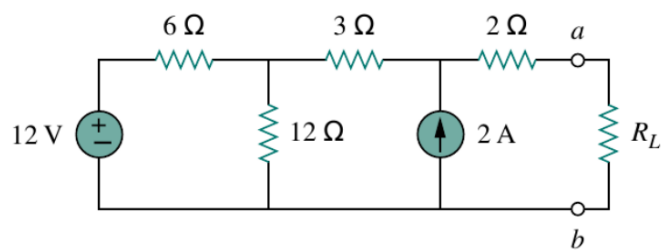4 - For the circuit given below find the value of R_L for maximum power transfer, also calculate the maximum power transferred



5- For the circuit given below, after staying on position 1 for a very long time, the position of the switch on the circuit is changed to 2 at time $t = 0$. Find the expressions for $i(t)$, $v(t)$ and $V_A(t)$ for $t > 0$.

